

# C & DS Assignment

ADYASA MOHANTY - EE18BTECH11048

Download codes from

<https://github.com/adyasa611/EE4013/tree/main/Assignment-1/codes>

and latex-tikz codes from

<https://github.com/adyasa611/EE4013/tree/main/Assignment-1/figures>

## 1 SOLVING A CIRCUIT PROBLEM USING GRAPH THEORY

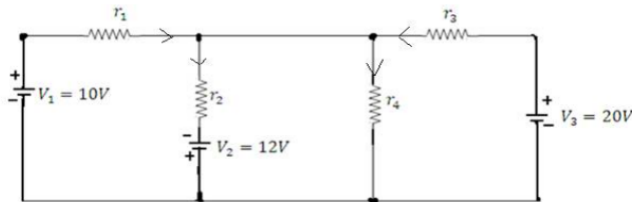


Fig. 0: Question

$$r_1 = 2\Omega, r_2 = 5\Omega, r_3 = 1\Omega, r_4 = 10\Omega$$

## 2 THEORY

### 2.1 Fundamental Tie Set Matrix (Fundamental Loop Matrix)

- 1) We define the edges of the graph and remove all the elements like voltage source, resistor, capacitor from the circuit and the corresponding graph is formed.
- 2) The graph has loops, we define and number the edges and the non overlapping loops and give a direction for current flow in each loop.
- 3) We then form a matrix with n (number of edges) rows and m (number of loops) columns.
- 4) We check if an edge is a part of the loop or not, if it is not then we assign 0 in the respective cell.
- 5) If edge is part of the loop, we check the direction of loop and current flow. If they coincide we assign the value 1 in the cell, else -1.
- 6) This is the Fundamental Tie Set Matrix, denoted by B.

### 2.2 KVL & KCL

- 1) KVL states that for a closed loop series path the algebraic sum of all the voltages around any closed loop in a circuit is equal to zero.
- 2) In the matrix form it can be represented as  $BV_b=0$  where  $V_b$  vector represents the total voltage drop in each branch of the circuit(edge).
- 3)  $V_b = V_s + Z_b I_b$  where  $V_s, Z_b, I_b$  are matrices and vectors
- 4)  $V_s =$  Voltage Source,  $I_b =$  Current in that branch,  $Z_b =$  Impedance of that branch.
- 5)  $B(V_s + Z_b I_b) = 0$
- 6)  $B(Z_b I_b) = -BV_s$
- 7) From KCL we know that  $I_b = B^T I_L$  where  $B^T$  is the transpose of B and  $I_L$  is the current in each loop.
- 8) So,  $BZ_b B^T I_L = -BV_s$

## 3 SOLUTION FOR GIVEN CIRCUIT

- 1) The graph for the given circuit can be represented as:

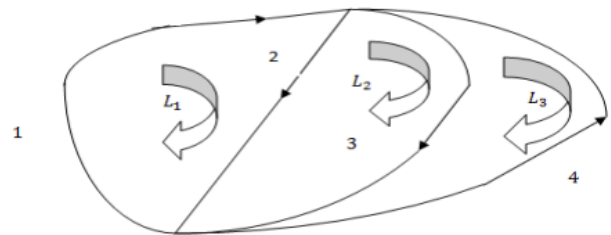


Fig. 1: Loops and Current Flow

- 2) We have to define the parameters

$$B = \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & -1 \end{bmatrix}$$

$$Z_b = \begin{bmatrix} 2 & 0 & 0 & 0 \\ 0 & 5 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 10 \end{bmatrix}$$

$$V_s = \begin{bmatrix} 10 \\ 12 \\ 0 \\ 20 \end{bmatrix}$$

$$I_L = \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$

3) We put these parameters in the equation :  $BZ_bB^T I_L = -BV_s$

4) We can solve this using pen and paper or using a basic code.

Python code to solve the above equation.

codes/Circuit.py

5) The current values are  $I_L = \begin{bmatrix} -3.72\text{A} \\ -0.8\text{A} \\ 1.74\text{A} \end{bmatrix}$

6) The negative sign indicates that our assumption of current flow direction was wrong.